

[Worldwide DX Amateur Radio Forums - Ham - CB - HF - VHF - UHF](#) > [Amateur Radio Related](#) > [Amplifiers](#)  
 **Quick and Dirty Class "AB" mod for KL300p**

**Welcome, [Klondike Mike](#).**  
You last visited: 02-22-2011 at 09:42 AM  
[Private Messages](#): Unread 0, Total 28.

[Home](#) [User CP](#) [FAQ](#) [Community](#) [Member Map](#) [New Posts](#) [Search](#) [Quick Links](#) [Satellite Maps](#) [DXSpot Map](#) [Chat Room](#) [Log Out](#)

#### Notices

Click [HERE](#) to find out how to enter the 2011 Spring Giveaway Contest!

#### Amateur Callsign Lookup


Enter Callsign:

## Quick and Dirty Class "AB" mod for KL300p

 [Post Reply](#)


 [View First Unread](#)

[LinkBack](#) [Thread Tools](#)

 02-22-2011, 03:41 PM

**[eagle1911](#)** 

Junior Member

 iTrader: (0)

#### Quick and Dirty Class "AB" mod for KL300p

This is a "quick and dirty" class AB mod for the KL300p that I ran across some time ago. While this providing a small bias source can be applied to just about any class C amp. Basically any amp that is class C. In this case, the inductor is part of the input transformer.

Procedure: First I used a dremel tool to carve a notch all the way around the outside end (closest to transformer, which is the smaller of the two transformers on the amp PCB. This disconnects the trace completely through the ground trace all the way around that end of the transformer. If you check for ohms. If you get a reading of 0 ohms, recheck to make sure that you've cut completely through the transformer.

I used a large 10W 100ohm resistor in line as well, one end of which I connected to the "Pre + Lin" pin. When the switch is on, this pin is a source of 13.8V. This way, the bias is only supplied if the amp is supplied to the transistors, and it is connected in series with a large 3A silicon diode (1N5402), the other end of the SD1446s (there is thermal paste between the two) and the cathode end (stripe) is connected to the emitter tabs. As you may already know a diode is simply a PN junction, and so this diode limits the voltage across the PN junction, generally .6-.7V depending on the junction temperature. At the connection point between the diode and the resistor, connect to the base of the first transistor (the one closest to the input transformer, on the same side as the cut that was made with the dremel. This replaces the original bias supply. This completes the rudimentary bias supply. This small voltage applied to the bases (.6-.7V) all times, which means your amp is now class AB. Since the components used are fairly heavy-duty, you don't have to worry about things moving around much.

This is a quick and dirty mod, partly due to limited room, and partly due to my feelings that simplicity. I see this same basic supply frequently in many 10-11m amps and even some Mirage VHF amps that give very similar results to many major name manufacturer's amps and most other simple class AB amps. Due to the physical arrangement of the diode and transistor you're actually a step ahead of many manufacturers.

There are much more complex bias designs out there that are meant to make sure the transistors are

of condition .. so if you really wanted to you could go much further with it and get even better results. Avoid overdriving the amp can help ensure that there is a reduction in the amount of distortion produced or fuzzy output then this mod might be just the thing you need.

Here's a pic of the end result:



Anyway, I just thought folks here might like to have a good description and pic of this mod, since I am not an expert in amp classes in general and how they are applied in real-world hardware.. this might help remove some of the confusion there with KL300p's that want cleaner SSB output and less distortion this will likely help them out too.

Last edited by eagle1911; 02-22-2011 at 04:50 PM.



02-22-2011, 04:38 PM

**bob85**

Senior Member



iTrader: (0)



whenever i use a diode to track temp i like to sand a flat on the diode to improve thermal contact, its good to see somebody out here doing some biasing

tom bearden taught me that quantum entanglement allows thought to travell faster than the speed of light, this explains a lot. wait a while you will see they are not very bright at all.



02-22-2011, 04:47 PM

**eagle1911**

Junior Member



iTrader: (0)



👍 That's actually a great idea, thanks! Never occurred to me to do that..



📅 02-22-2011, 05:24 PM

### **Shockwave**

Senior Member



iTrader: ([0](#))



I do see one problem with this basic mod that is easy to correct. The center tap on the input transfo That's not right. It should only be isolated from DC ground and returned to RF ground trough an ap ceramic cap between the two points cut with the Dremel. Keep the wires on the cap short to reduce



📅 02-22-2011, 05:35 PM

### **eagle1911**

Junior Member



iTrader: ([0](#))



Wow.. you guys are good! I'll add that to mine in the next few days and update the OP here with a



📅 02-22-2011, 07:11 PM



### **mackmobile43**

33 more than 43



iTrader: ([2](#))



Nice job there Eagle.

Ain't no feelin like mackmobeelin



📅 02-22-2011, 08:27 PM

### **eagle1911**

Junior Member




iTrader: ([0](#))



Tnx!

Well, it looks like I can't edit the OP anymore, so here's a new pic. Per Shockwave's observation (m the input transformer and the circular ground pad around the hole just next to it. As Shockwave sai ground as far as the DC bias voltage is concerned, while still providing a path to ground for the inco

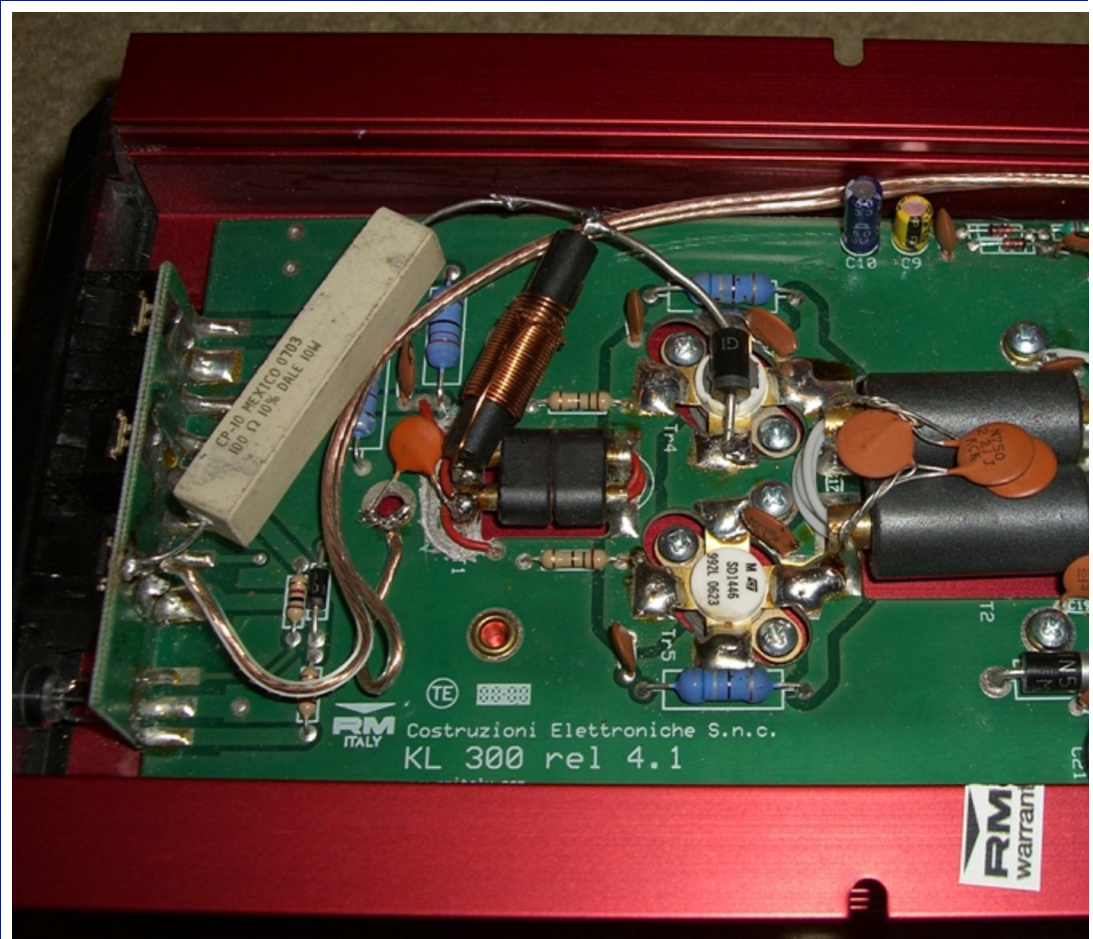The wire with clear insulation powers a fan I've mounted on the heatsink. The fan's positive wire is and the negative wire is connected to the same ground as the capacitor described above.



Last edited by eagle1911; 02-22-2011 at 08:40 PM.



[Post Reply](#)

#### Bookmarks



Digg



del.icio.us



StumbleUpon

#### Tags

None



Picture Product



[VINTAGE HEATHKIT IMPEDANCE BRIDGE.](#)



[Heathkit HA 10 amplifier](#)



[HEATHKIT 2-METER FM AMPLIFIER AMP HAM RADIO HA-202A](#)

[View all 10 items on eBay](#)



Price Picture Product



\$11.86

[Ameritron 600 Power Supply -](#)



\$56.99

[Ameritron AL-8 Amplifier](#)



\$9.89


[AMERITRON AL-8 AMPLIFIER EX](#)


[disclaimer](#)


[View all 5 items on eBay](#)


### Quick Reply


Message:

**B***I***U**









Options

☐ Quote message in reply?

Post Quick Reply

Go Advanced

« [A Very Rare Find...](#) | - »

**Currently Active Users Viewing This Thread: 2** (2 members and 0 guests)

**Klondike Mike**, [eagle1911](#)

#### Posting Rules

You **may** post new threads  
You **may** post replies  
You **may** post attachments  
You **may** edit your posts

[BB code](#) is **On**  
[Smilies](#) are **On**  
[\[IMG\]](#) code is **On**  
HTML code is **Off**  
[Trackbacks](#) are **On**  
[Pingbacks](#) are **On**  
[Refbacks](#) are **On**

[Forum Rules](#)

For

All times are GMT -7. The time now is 08:45 PM.

[Contact Us](#) - [Worldwide DX Amateur Radio Forums](#) - [Ham](#) - [CB](#) - [HF](#) - [VHF](#) - [UHF](#) - [Top](#)

Powered by vBulletin®  
Copyright ©2000 - 2011, Jelsoft Enterprises Ltd.  
Search Engine Optimization by [vBSEO](#) 3.5.2  
Worldwide Radio Forum